

Digital Circuits

Cezar Ionescu
cezar.ionescu@th-deg.de

WS 2023-24



Outline

- 1 Admin
- 2 Review
- 3 Digital gates

Admin

Questions?

Review

Binary arithmetic

- Addition (carry is 0 or 1):

```
  1111      (carry)
  10110
+01110
-----
 100100
```

- Multiplication

```
   1110
x  1001
-----
   1110
  0000
 0000
1110
-----
1111110
```

Digital gates

- **Fundamental insight:** arithmetical operations on many large numbers can be decomposed into a (large) number of standard operations on few small numbers.
- Example:
 - $a_1 + a_2 + \dots + a_n = a_1 + (a_2 + (a_3 + (\dots + a_n) \dots))$

Decomposing addition in base b

$$\begin{array}{cccc} & [x_1 & x_2 & \dots & x_n] \\ + & [y_1 & y_2 & \dots & y_n] \\ [z_0 & z_1 & z_2 & \dots & z_n] \end{array} =$$

where

$$c_k = \text{if } k == n \text{ then } 0 \text{ else } x_{k+1} + y_{k+1} + c_{k+1} \text{ div } b$$

$$z_k = \text{if } k == 0 \text{ then } c_0 \text{ else } x_k + y_k + c_k \text{ mod } b$$

Decomposing addition in base 2

For base 2, obtaining the results

$$c_k = \text{if } k == n \text{ then } 0 \text{ else } x_{k+1} + y_{k+1} + c_{k+1} \text{ div } b$$

$$z_k = \text{if } k == 0 \text{ then } c_0 \text{ else } x_k + y_k + c_k \text{ mod } b$$

involves examining only one or two *bits* at a time.

One-bit operations

Let $\mathbb{B} = \{0, 1\}$.

How many non-constant functions of type $\mathbb{B} \rightarrow \mathbb{B}$ are there?

One-bit operations

Let $\mathbb{B} = \{0, 1\}$.

How many non-constant functions of type $\mathbb{B} \rightarrow \mathbb{B}$ are there?

Two:

id 0 = 0

id 1 = 1

neg 0 = 1

neg 1 = 0

Identity

Implementing the identity function is trivial:




Negation

The *negate* function (also known as flip, invert, change, reverse, etc.) is usually denoted by \neg , \neg , or $\bar{\cdot}$ and has the truth table

x	\bar{x}
0	1
1	0

and is implemented by a NOT gate:

 

Two-bit operations

How many functions of type $\mathbb{B} \times \mathbb{B} \rightarrow \mathbb{B}$ are there?

```
const1 (b_1, b_2) = 1
```

```
min (b_1, b_2)    = if b_1 == 0 or b_2 == 0 then 0 else 1
```

```
max (b_1, b_2)    = if b_1 == 1 or b_2 == 1 then 1 else 0
```

```
leq (b_1, b_2)    = if b_1 == 0 then 1 else b_2
```

Two-bit operations

How many functions of type $\mathbb{B} \times \mathbb{B} \rightarrow \mathbb{B}$ are there?

$$2^4 = 16$$

Examples:

```
const0 (b_1, b_2) = 0
```

```
const1 (b_1, b_2) = 1
```

```
min (b_1, b_2)    = if b_1 == 0 or b_2 == 0 then 0 else 1
```

```
max (b_1, b_2)    = if b_1 == 1 or b_2 == 1 then 1 else 0
```

```
leq (b_1, b_2)    = if b_1 == 0 then 1 else b_2
```


Two-bit operations

How many functions of type $\mathbb{B} \times \mathbb{B} \rightarrow \mathbb{B}$ are there?

$$2^4 = 16$$

Examples:

```
const0 (b_1, b_2) = 0
```

```
const1 (b_1, b_2) = 1
```

```
min (b_1, b_2)    = if b_1 == 0 or b_2 == 0 then 0 else 1
```

```
max (b_1, b_2)    = if b_1 == 1 or b_2 == 1 then 1 else 0
```

```
leq (b_1, b_2)    = if b_1 == 0 then 1 else b_2
```

Two-bit operations

How many functions of type $\mathbb{B} \times \mathbb{B} \rightarrow \mathbb{B}$ are there?

$$2^4 = 16$$

Examples:

```
const0 (b_1, b_2) = 0
```

```
const1 (b_1, b_2) = 1
```

```
min (b_1, b_2)    = if b_1 == 0 or b_2 == 0 then 0 else 1
```

```
max (b_1, b_2)    = if b_1 == 1 or b_2 == 1 then 1 else 0
```

```
leq (b_1, b_2)    = if b_1 == 0 then 1 else b_2
```

Two-bit operations

How many functions of type $\mathbb{B} \times \mathbb{B} \rightarrow \mathbb{B}$ are there?

$$2^4 = 16$$

Examples:

```
const0 (b_1, b_2) = 0
```

```
const1 (b_1, b_2) = 1
```

```
min (b_1, b_2)    = if b_1 == 0 or b_2 == 0 then 0 else 1
```

```
max (b_1, b_2)    = if b_1 == 1 or b_2 == 1 then 1 else 0
```

```
leq (b_1, b_2)    = if b_1 == 0 then 1 else b_2
```

Interpretation of bit operations

Function of type $\mathbb{B}^n \rightarrow \mathbb{B}$ have several interpretations:

- as restrictions of functions of type $\mathbb{N}^n \rightarrow \mathbb{N}$
 - in particular, we have that $1 + 1 = 2$, therefore $+$ is *not* such a function
- as functions on numbers *modulo* 2 ($\mathbb{B} = \mathbb{Z}_2$)
 - in particular, we have that $1 + 1 = 0$
- as functions on *truth values* ($\mathbb{B} = \{\text{False}, \text{True}\}$)
 - example, $+$ on \mathbb{Z}_2 above corresponds to the logical function xor

The standard terminology favours the “logical” interpretation.

Interpretation of bit operations

Function of type $\mathbb{B}^n \rightarrow \mathbb{B}$ have several interpretations:

- as restrictions of functions of type $\mathbb{N}^n \rightarrow \mathbb{N}$
 - in particular, we have that $1 + 1 = 2$, therefore $+$ is *not* such a function
- as functions on numbers *modulo* 2 ($\mathbb{B} = \mathbb{Z}_2$)
 - in particular, we have that $1 + 1 = 0$
- as functions on *truth values* ($\mathbb{B} = \{\text{False}, \text{True}\}$)
 - example, $+$ on \mathbb{Z}_2 above corresponds to the logical function xor

The standard terminology favours the “logical” interpretation.

Interpretation of bit operations

Function of type $\mathbb{B}^n \rightarrow \mathbb{B}$ have several interpretations:

- as restrictions of functions of type $\mathbb{N}^n \rightarrow \mathbb{N}$
 - in particular, we have that $1 + 1 = 2$, therefore $+$ is *not* such a function
- as functions on numbers *modulo* 2 ($\mathbb{B} = \mathbb{Z}_2$)
 - in particular, we have that $1 + 1 = 0$
- as functions on *truth values* ($\mathbb{B} = \{\text{False}, \text{True}\}$)
 - example, $+$ on \mathbb{Z}_2 above corresponds to the logical function xor

The standard terminology favours the “logical” interpretation.

Interpretation of bit operations

Function of type $\mathbb{B}^n \rightarrow \mathbb{B}$ have several interpretations:

- as restrictions of functions of type $\mathbb{N}^n \rightarrow \mathbb{N}$
 - in particular, we have that $1 + 1 = 2$, therefore $+$ is *not* such a function
- as functions on numbers *modulo* 2 ($\mathbb{B} = \mathbb{Z}_2$)
 - in particular, we have that $1 + 1 = 0$
- as functions on *truth values* ($\mathbb{B} = \{\text{False}, \text{True}\}$)
 - example, $+$ on \mathbb{Z}_2 above corresponds to the logical function xor



The standard terminology favours the “logical” interpretation.

The AND gate

The and function should probably be better called min, and is usually denoted by \wedge , \cdot , or just juxtaposition (as we normally do in the case of multiplication). The truth table is

x	y	xy
0	0	0
0	1	0
1	0	0
1	1	1

and is implemented by an AND gate:

  



(<https://commons.wikimedia.org/wiki/File:TransistorANDgate.png>)

The OR gate

The or function should probably be better called max, and is usually denoted by \vee , $|$, or $+$. The truth table is

x	y	$x+y$
0	0	0
0	1	1
1	0	1
1	1	1

and is implemented by an OR gate:

  



(https://commons.wikimedia.org/wiki/File:Transistor\OR_Gate.png)

The XOR gate

The xor function should probably be better called not equal, and is usually denoted by \oplus . The truth table is

x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

and is implemented by an XOR gate:

  

(<https://commons.wikimedia.org/wiki/File:TransmissionCmosXORGate.png>)

Digital: digital logic designer and simulator

Digital

Implementing XOR

Exercise: implement XOR in Digital, using NOT, AND, and OR gates.

Implementing OR


Exercise: implement OR in Digital, using NOT and AND gates.

The NAND gate


The truth table of the nand function is:

x	y	x nand y
0	0	1
0	1	1
1	0	1
1	1	0

and is implemented by a NAND gate:

 

PMOS NAND gate

 

Implementing NAND

Exercise: implement NAND using NOT and AND gates.

Implementing using NAND

Exercise: implement the NOT, AND, and OR gates using only NAND gates.

Sum-of-terms expressions for boolean functions

Consider the truth table of a boolean function f of n variables:

x_1	x_2	...	x_n	$f(x_1, x_2, \dots, x_n)$
0	0	...	0	$f(0, 0, \dots, 0)$
0	0	...	1	$f(0, 0, \dots, 1)$
...
1	1	1	1	$f(1, 1, \dots, 1)$

Each row of the table can be described by a *minterm*, a conjunction of the variables in which the variables corresponding to 0s are negated. Thus, the minterm corresponding to row r is

r_{th} minterm = $b_1 b_2 \dots b_n$ where
 $b_i = x_i$, if $x_i = 1$ in the r_{th} row
 $= \neg x_i$, otherwise

A formula for f is then given by the *disjunction* of minterms corresponding to rows in which f has the value 1. A formula in this form is called a *sum-of-terms* expression.

Sum-of-terms expressions for boolean functions

Consider the truth table of a boolean function f of n variables:

x_1	x_2	...	x_n	$f(x_1, x_2, \dots, x_n)$
0	0	...	0	$f(0, 0, \dots, 0)$
0	0	...	1	$f(0, 0, \dots, 1)$
...
1	1	1	1	$f(1, 1, \dots, 1)$

Each row of the table can be described by a *minterm*, a conjunction of the variables in which the variables corresponding to 0s are negated. Thus, the minterm corresponding to row r is

r_{th} minterm = $b_1 b_2 \dots b_n$ where
 $b_i = x_i$, if $x_i = 1$ in the r_{th} row
 $= \neg x_i$, otherwise

A formula for f is then given by the *disjunction* of minterms corresponding to rows in which f has the value 1. A formula in this form is called a *sum-of-terms* expression.

Sum-of-terms expressions for boolean functions

Consider the truth table of a boolean function f of n variables:

x_1	x_2	...	x_n	$f(x_1, x_2, \dots, x_n)$
0	0	...	0	$f(0, 0, \dots, 0)$
0	0	...	1	$f(0, 0, \dots, 1)$
...
1	1	1	1	$f(1, 1, \dots, 1)$

Each row of the table can be described by a *minterm*, a conjunction of the variables in which the variables corresponding to 0s are negated. Thus, the minterm corresponding to row r is

r_{th} minterm = $b_1 b_2 \dots b_n$ where
 $b_i = x_i$, if $x_i = 1$ in the r_{th} row
 $= \neg x_i$, otherwise

A formula for f is then given by the *disjunction* of minterms corresponding to rows in which f has the value 1. A formula in this form is called a *sum-of-terms* expression.

Example

Find a sum-of-terms expression for the boolean function

$$\begin{aligned}f(x_1, x_2, x_3) &= 1, \text{ if } x_1 < x_3 \\ &= 0, \text{ otherwise}\end{aligned}$$

Solution:

x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$$f(x_1, x_2, x_3) = \overline{x_1} \overline{x_2} x_3 + \overline{x_1} x_2 x_3$$

Example

Find a sum-of-terms expression for the boolean function

$$\begin{aligned} f(x_1, x_2, x_3) &= 1, \text{ if } x_1 < x_3 \\ &= 0, \text{ otherwise} \end{aligned}$$

Solution:

x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$$f(x_1, x_2, x_3) = \overline{x_1} \overline{x_2} x_3 + \overline{x_1} x_2 x_3$$

Properties of boolean operations

Boolean operations have a number of properties, similar (but not identical) to the familiar arithmetic ones:

- *commutativity*: $xy = yx$, $x + y = y + x$
- *associativity*: $x(yz) = (xy)z$, $x + (y + z) = (x + y) + z$
- *distributivity*: $x(y + z) = xy + xz$, $x + yz = (x + y)(x + z)$ (!)
- *idempotence*: $xx = x$, $x + x = x$
- *unit elements*: $x1 = x$, $x + 0 = x$
- *duality (de Morgan)*: $\overline{(x + y)} = \bar{x} \bar{y}$, $\overline{xy} = \bar{x} + \bar{y}$
- *inverses*: $x + \bar{x} = 1$ (*law of excluded middle*), $x\bar{x} = 0$ (*law of contradiction*), $\bar{\bar{x}} = x$ (*law of double negation*)

Simplifying boolean expressions

The properties of boolean operations can be used to simplify expressions, which can translate in more efficient implementations.

Example: simplify the expression obtained for f above. **Solution:**

$$\begin{aligned} & \overline{x_1} \overline{x_2} x_3 + \overline{x_1} x_2 x_3 \\ = & \quad \{commutativity, associativity\} \\ & \overline{x_1} x_3 \overline{x_2} + \overline{x_1} x_3 x_2 \\ = & \quad \{distributivity\} \\ & \overline{x_1} x_3 (\overline{x_2} + x_2) \\ = & \quad \{excluded\ middle\} \\ & \overline{x_1} x_3 1 \\ = & \quad \{unit\} \\ & \overline{x_1} x_3 \end{aligned}$$

Simplifying boolean expressions

The properties of boolean operations can be used to simplify expressions, which can translate in more efficient implementations.

Example: simplify the expression obtained for f above. Solution:

$$\begin{aligned} & \overline{x_1} \overline{x_2} x_3 + \overline{x_1} x_2 x_3 \\ = & \quad \{commutativity, associativity\} \\ & \overline{x_1} x_3 \overline{x_2} + \overline{x_1} x_3 x_2 \\ = & \quad \{distributivity\} \\ & \overline{x_1} x_3 (\overline{x_2} + x_2) \\ = & \quad \{excluded\ middle\} \\ & \overline{x_1} x_3 1 \\ = & \quad \{unit\} \\ & \overline{x_1} x_3 \end{aligned}$$

Karnaugh maps

- *Karnaugh maps* are an alternative tabular representation of logical functions.
- In a Karnaugh map minterms that differ in only one variable are adjacent.
- The goal of using a Karnaugh map is to obtain the simplest sum of terms expression.
 - Karnaugh maps are an alternative to the equational form of simplification.

Karnaugh maps

- Let $f: \mathbb{B}^N \rightarrow \mathbb{B}$.
- Let R and C be such that
 - $R = C = N/2$, if N is even
 - $R + C = N$, $|R - C| = 1$, if N is odd
- We associate the variables x_1, \dots, x_R to the rows and x_{R+1}, \dots, x_N to the columns of the Karnaugh map.
- The Karnaugh map will have 2^R rows and 2^C columns. Each row is labelled with R bits and each column is labelled with C bits in *Gray code*.

Gray code

- The *Gray code* is a method of enumerating the 2^N possible binary numbers representable with N bits such that successive representations differ in *only one bit*.
- The enumeration can be seen as a table with N columns and 2^N rows.
- For $N = 1$, the table is just

0
1

- For $N > 1$, the table is obtained by taking the table for $N - 1$ and *reflecting* it across the last line. The result will then have $N - 1$ columns and 2^N rows. We extend this with a first column consisting of 2^{N-1} zeros, followed by 2^{N-1} ones.
- Example: $N = 2$

0		0		0	0
1	\Rightarrow	1	\Rightarrow	0	1
		1		1	1
		0		1	0

Gray code

- The *Gray code* is a method of enumerating the 2^N possible binary numbers representable with N bits such that successive representations differ in *only one bit*.
- The enumeration can be seen as a table with N columns and 2^N rows.
- For $N = 1$, the table is just

0
1

- For $N > 1$, the table is obtained by taking the table for $N - 1$ and *reflecting* it across the last line. The result will then have $N - 1$ columns and 2^N rows. We extend this with a first column consisting of 2^{N-1} zeros, followed by 2^{N-1} ones.
- Example: $N = 2$

0	⇒	0	⇒	0	0
1		1		0	1
		1		1	1
		0		1	0

Gray code

- The *Gray code* is a method of enumerating the 2^N possible binary numbers representable with N bits such that successive representations differ in *only one bit*.
- The enumeration can be seen as a table with N columns and 2^N rows.
- For $N = 1$, the table is just

0
1

- For $N > 1$, the table is obtained by taking the table for $N - 1$ and *reflecting* it across the last line. The result will then have $N - 1$ columns and 2^N rows. We extend this with a first column consisting of 2^{N-1} zeros, followed by 2^{N-1} ones.
- Example: $N = 2$

0	⇒	0	⇒	0	0
1		1		0	1
		1		1	1
		0		1	0

Gray code

- The *Gray code* is a method of enumerating the 2^N possible binary numbers representable with N bits such that successive representations differ in *only one bit*.
- The enumeration can be seen as a table with N columns and 2^N rows.
- For $N = 1$, the table is just

0
1

- For $N > 1$, the table is obtained by taking the table for $N - 1$ and *reflecting* it across the last line. The result will then have $N - 1$ columns and 2^N rows. We extend this with a first column consisting of 2^{N-1} zeros, followed by 2^{N-1} ones.
- Example: $N = 2$

0 0 0 0
1 \Rightarrow 1 \Rightarrow 0 1
 1 1 1
 0 1 0

Gray code

- The *Gray code* is a method of enumerating the 2^N possible binary numbers representable with N bits such that successive representations differ in *only one bit*.
- The enumeration can be seen as a table with N columns and 2^N rows.
- For $N = 1$, the table is just

0
1

- For $N > 1$, the table is obtained by taking the table for $N - 1$ and *reflecting* it across the last line. The result will then have $N - 1$ columns and 2^N rows. We extend this with a first column consisting of 2^{N-1} zeros, followed by 2^{N-1} ones.
- Example: $N = 2$

0		0		0	0
1	\Rightarrow	1	\Rightarrow	0	1
		1		1	1
		0		1	0

Gray code example

0	0	0
0	0	1
0	1	1
0	1	0
1	1	0
1	1	1
1	0	1
1	0	0

Karnaugh maps

- We associate the variables x_1, \dots, x_R to the rows and x_{R+1}, \dots, x_N to the columns of the Karnaugh map.
- The Karnaugh map will have 2^R rows and 2^C columns. Each row is labelled with R bits and each row is labelled with C bits in *Gray code*.
- We find *maximal* blocks of *adjacent 1s of size power of two*. The blocks may overlap, as long as they differ in at least one cell.
- The minterm associated to each block is given by the variables that remain constant across the block.
- The sum-of-terms expression is then the sum of the minterms.

Example

(source Wikipedia)

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	$f(A, B, C, D)$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

- 1 Derive the sum of terms expression from the truth table.
- 2 Derive a simplified sum-of-terms expression using the Karnaugh map representation of f .