

Implementing Binary Arithmetic

Cezar Ionescu
cezar.ionescu@th-deg.de

WS 2023-24



Outline

- 1 Admin
- 2 Review
- 3 Implementing binary arithmetic

Admin

Questions?

Review

Binary arithmetic

- Addition (carry is 0 or 1):

```
  1111      (carry)
  10110
+01110
-----
 100100
```

- Multiplication

```
   1110
x  1001
-----
   1110
  0000
 0000
1110
-----
1111110
```

- NOT, OR, AND, XOR, NAND, NOR
- sum-of-terms expressions
- Karnaugh maps

Implementing binary arithmetic

We follow Chapter 4 of *Foundations of Computer Science*, A.J.T. Colin, Macmillan 1980, which is also the source of the following images.

One-bit addition

- Addition on natural numbers is a function of type $\mathbb{N} \times \mathbb{N} \rightarrow \mathbb{N}$.
 - If $n + n = 0$, then $n = 0$
- If we consider addition on \mathbb{B} to be of the analog type $\mathbb{B} \times \mathbb{B} \rightarrow \mathbb{B}$, we have a loss of information:
 - $1 + 1 = 0$ (therefore $1 = 0$?)
- To avoid loss of information, we can extend the output type: $\mathbb{B} \times \mathbb{B} \rightarrow \mathbb{B} \times \mathbb{B}$
 - $1 + 1 = (0, 1) \neq 0$
 - alternative notation:

```
add05 : B2 -> B2
add05 (x, y) = (sum, carry)
where sum    = (x + y) mod 2
      carry  = (x + y) div 2
```
- This function is called **half-adder**.

One-bit addition

- Addition on natural numbers is a function of type $\mathbb{N} \times \mathbb{N} \rightarrow \mathbb{N}$.
 - If $n + n = 0$, then $n = 0$
- If we consider addition on \mathbb{B} to be of the analog type $\mathbb{B} \times \mathbb{B} \rightarrow \mathbb{B}$, we have a loss of information:
 - $1 + 1 = 0$ (therefore $1 = 0$?)
- To avoid loss of information, we can extend the output type: $\mathbb{B} \times \mathbb{B} \rightarrow \mathbb{B} \times \mathbb{B}$
 - $1 + 1 = (0, 1) \neq 0$
 - alternative notation:

```
add05 : B2 -> B2
add05 (x, y) = (sum, carry)
where sum    = (x + y) mod 2
      carry  = (x + y) div 2
```
- This function is called **half-adder**.

One-bit addition

- Addition on natural numbers is a function of type $\mathbb{N} \times \mathbb{N} \rightarrow \mathbb{N}$.
 - If $n + n = 0$, then $n = 0$
- If we consider addition on \mathbb{B} to be of the analog type $\mathbb{B} \times \mathbb{B} \rightarrow \mathbb{B}$, we have a loss of information:
 - $1 + 1 = 0$ (therefore $1 = 0$?)
- To avoid loss of information, we can extend the output type: $\mathbb{B} \times \mathbb{B} \rightarrow \mathbb{B} \times \mathbb{B}$
 - $1 + 1 = (0, 1) \neq 0$
 - alternative notation:

```
add05 : B2 -> B2  
add05 (x, y) = (sum, carry)  
where sum    = (x + y) mod 2  
        carry = (x + y) div 2
```

- This function is called **half-adder**.

One-bit addition

- Addition on natural numbers is a function of type $\mathbb{N} \times \mathbb{N} \rightarrow \mathbb{N}$.
 - If $n + n = 0$, then $n = 0$
- If we consider addition on \mathbb{B} to be of the analog type $\mathbb{B} \times \mathbb{B} \rightarrow \mathbb{B}$, we have a loss of information:
 - $1 + 1 = 0$ (therefore $1 = 0$?)
- To avoid loss of information, we can extend the output type: $\mathbb{B} \times \mathbb{B} \rightarrow \mathbb{B} \times \mathbb{B}$
 - $1 + 1 = (0, 1) \neq 0$
 - alternative notation:

```
add05 : B2 -> B2  
add05 (x, y) = (sum, carry)  
where sum    = (x + y) mod 2  
        carry = (x + y) div 2
```

- This function is called **half-adder**.

One-bit addition

- $\text{add}_{05} : B^2 \rightarrow B^2$
 $\text{add}_{05}(x, y) = (\text{sum}, \text{carry})$
where $\text{sum} = (x + y) \bmod 2$
 $\text{carry} = (x + y) \text{div } 2$
- We want to use add_{05} to add two-digit binary numbers, e.g. $01 + 11$

```
  0 1
  1 1
-----
c1r1r0
```

$\text{add}_{05}(1, 1) = (\text{sum}_0, \text{car}_0) = (0, 1) \text{ -- ok}$

$\text{add}_{05}(0, 1) = (\text{sum}_1, \text{car}_1) = (1, 0) \text{ -- ok}$

But the result is not $\text{car}_1 \text{sum}_1 \text{sum}_0 = [1, 0]$ (first element of the results of add_{05}), because we've lost car_0 .

One-bit addition

- $\text{add}_{05} : \mathbf{B^2} \rightarrow \mathbf{B^2}$
 $\text{add}_{05} (x, y) = (\text{sum}, \text{carry})$
where $\text{sum} = (x + y) \bmod 2$
 $\text{carry} = (x + y) \text{div } 2$
- We want to use add_{05} to add two-digit binary numbers, e.g. $01 + 11$

```
  0 1
  1 1
-----
c1r1r0
```

$\text{add}_{05}(1, 1) = (\text{sum}_0, \text{car}_0) = (0, 1) \text{ -- ok}$

$\text{add}_{05}(0, 1) = (\text{sum}_1, \text{car}_1) = (1, 0) \text{ -- ok}$

But the result is not $\text{car}_1\text{sum}_1\text{sum}_0 = [1, 0]$ (first element of the results of add_{05}), because we've lost car_0 .

One-bit addition

- $\text{add}_{05} : B^2 \rightarrow B^2$
 $\text{add}_{05}(x, y) = (\text{sum}, \text{carry})$
where $\text{sum} = (x + y) \bmod 2$
 $\text{carry} = (x + y) \text{div } 2$
- We want to use add_{05} to add two-digit binary numbers, e.g. $01 + 11$

```
  0 1
  1 1
-----
c1r1r0
```

$\text{add}_{05}(1, 1) = (\text{sum}_0, \text{car}_0) = (0, 1) \text{ -- ok}$

$\text{add}_{05}(0, 1) = (\text{sum}_1, \text{car}_1) = (1, 0) \text{ -- ok}$

But the result is not $\text{car}_1 \text{sum}_1 \text{sum}_0 = [1, 0]$ (first element of the results of add_{05}), because we've lost car_0 .

One-bit addition

To accomodate the carry, we need to extend the input type as well.

$\text{add}_1 : \mathbf{B^3} \rightarrow \mathbf{B^2}$

$\text{add}_1(x, y, c_0) = (\text{sum}, \text{carry})$ **where**

$\text{sum} = (x + y + c_0) \bmod 2$

$\text{carry} = (x + y + c_0) \text{div } 2$

Example: Using add_1 to implement *two-bit* addition.

$a_1a_0 + b_1b_0 = c_1s_1s_0$ where

$(s_0, c_0) = \text{add}_1(a_0, b_0, 0)$ -- initial carry is 0

$(s_1, c_1) = \text{add}_1(a_1, b_1, c_0)$ -- intermediate carry is c_0

One-bit addition

To accomodate the carry, we need to extend the input type as well.

$\text{add}_1 : B^3 \rightarrow B^2$

$\text{add}_1(x, y, c_0) = (\text{sum}, \text{carry})$ where

$\text{sum} = (x + y + c_0) \bmod 2$

$\text{carry} = (x + y + c_0) \text{div } 2$

Example: Using add_1 to implement *two-bit* addition.

$a_1a_0 + b_1b_0 = c_1s_1s_0$ where

$(s_0, c_0) = \text{add}_1(a_0, b_0, 0)$ -- initial carry is 0


$(s_1, c_1) = \text{add}_1(a_1, b_1, c_0)$ -- intermediate carry is c_0

Implementing one-bit addition

x	y	c	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

The one-bit adder

 A one-bit adder is a circuit that implements one-bit addition. For example



Alternative implementation

The half-adder function can also be used to implement a one-bit adder:

$\text{add}_1(x, y, c_0) = (\text{sum}, \text{carry})$ **where**

$$\begin{aligned}(s_1, c_1) &= \text{add}_{05}(x, y) \\ (\text{sum}, c_2) &= \text{add}_{05}(s_1, c_0) \\ \text{carry} &= c_1 \text{ OR } c_2\end{aligned}$$

The advantage of this formulation is that the half-adder is a very simple circuit to implement:

$\text{add}_{05}(x, y) = (x \text{ XOR } y, x \text{ AND } y)$

Alternative implementation

The half-adder function can also be used to implement a one-bit adder:


```
add1 (x, y, c0) = (sum, carry) where  
  (s1, c1) = add05(x, y)  
  (sum, c2) = add05(s1, c0)  
  carry    = c1 OR c2
```

The advantage of this formulation is that the half-adder is a very simple circuit to implement:

```
add05(x, y) = (x XOR y, x AND y)
```

Block representation of a one-bit adder

 We can represent the one-bit adder as a *black box*, hiding the implementation:



Four-bit adders

$\text{add}_4(x_3x_2x_1x_0, y_3y_2y_1y_0) = c_3s_3s_2s_1s_0$

$(s_0, c_0) = \text{add}_1(x_0, y_0, 0)$ -- initial carry is 0


$(s_1, c_1) = \text{add}_1(x_1, y_1, c_0)$

$(s_2, c_2) = \text{add}_1(x_2, y_2, c_1)$

$(s_3, c_3) = \text{add}_1(x_3, y_3, c_2)$

Four-bit adders


Implementation:

 

Four-bit systems

In an n -bit system, circuits will usually work on groups of n bits in size (plus the occasional *control* bits like the carry).

 Therefore, a more compact representation is adopted for such groups. For example:



This is similar to the introduction of vectors in linear algebra, allowing us to use $\mathbf{x} \in \mathbb{R}^n$ to represent (x_{n-1}, \dots, x_0) , $x_i \in \mathbb{R}$.


Subtraction on n bit numbers

- Let xs and ys be n bit numbers. Then


$$xs - ys = xs + (-ys) = xs + (\text{flip}_n(ys) + 1)$$

where flip_n inverts every bit of an n bit input.

Implementing two's complement

 

Implementing subtraction

 

The multiplexer


The two-way multiplexer selects one of the two input lines depending on the value of the control input (sel).

sel	x	y	out
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

A more compact description of the multiplexer:

sel	out
0	x
1	y

Implementing a multiplexer

 

A four-way multiplexer


We can also build multiplexers that select one of more than two (usually 2^n) alternatives. In this case, we need more than one bit to represent the selection. For example, a four-way multiplexer selects one out of four signals u , v , x , y .

sel_0	sel_1	out
0	0	u
0	1	v
1	0	x
1	1	y

Shifting binary numbers

- Given a binary number $x_1x_2\dots x_n$, the operation *left shift* produces the (truncated) result of the multiplication with 2: $x_2x_3\dots x_n0$.
- Similarly, the *right shift* produces the (truncated) result of dividing the number by 2: $0x_1x_2\dots x_{n-1}$.

An arithmetic unit

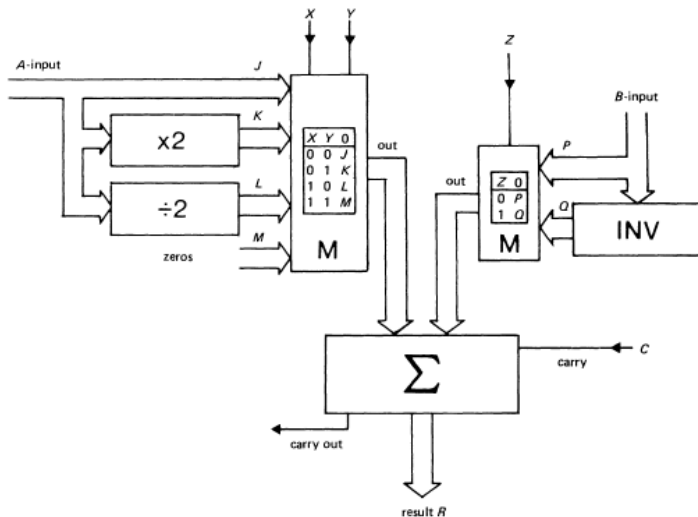

Functionality table

X	Y	Z	C	Effective function
0	0	0	0	$R = A + B$
0	0	0	1	$R = A + B + 1$
0	0	1	0	$R = A - B - 1$
0	0	1	1	$R = A - B$
0	1	0	0	$R = 2A + B$
0	1	0	1	$R = 2A + B + 1$
0	1	1	0	$R = 2A - B - 1$
0	1	1	1	$R = 2A - B$
1	0	0	0	$R = \frac{1}{2}A + B$
1	0	0	1	$R = \frac{1}{2}A + B + 1$
1	0	1	0	$R = \frac{1}{2}A - B - 1$
1	0	1	1	$R = \frac{1}{2}A - B$
1	1	0	0	$R = B$
1	1	0	1	$R = B + 1$
1	1	1	0	$R = B - 1$
1	1	1	1	$R = B$