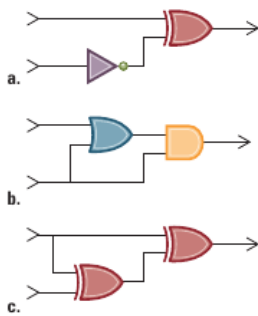


Problem Sheet: Digital Circuits


Cezar Ionescu

WS 2023-24


1. Define the truth table for the following circuits:



(e)

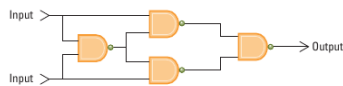

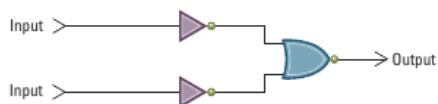2. (a) Give the truth table for the counterpart *nor* of the *nand* gate (a better name for *nor* would be *negmax*).
- (b) Implement *nor* using the standard gates (*not*, *and*, *or*).
- (c) Implement *nor* using only *nand* gates.
- (d) Implement the standard gates using only *nor* gates.
- (e) *Nor* gates are represented in the same way as *or* gates, except for having a circle at their output. Give the truth table for the following circuit:



3. Derive the simplest possible sum-of-terms expressions for each of the following functions

- (a) $f : \mathbb{B}^5 \rightarrow \mathbb{B}$, $f(x) = 1$ if x is the binary representation of a number between 20 and 30, and 0 otherwise
- (b) $f : \mathbb{B}^3 \rightarrow \mathbb{B}$, $f(x) = 1$ if there are more 1s than 0s in x
- (c) same as the previous one, but for $f : \mathbb{B}^4 \rightarrow \mathbb{B}$
- (d) $f : \mathbb{B}^4 \rightarrow \mathbb{B}$, $f(x) = 0$ if the number represented by x is even
- (e) $f : \mathbb{B}^4 \rightarrow \mathbb{B}$, $f(x_0, x_1, x_2, x_3) = 1$ if the number represented by x_0x_1 is smaller than x_2x_3 .
- (f) same as the previous one, but with “smaller than equal”.

4. Construct Karnaugh maps for each of the following expressions, and derive simplified versions:

- (a) $w\bar{x}\bar{y} + w\bar{x}y + \bar{w}xy + \bar{w}x\bar{y} + wxy + w\bar{x}y$
- (b) $w\bar{x}\bar{y} + \bar{w}x\bar{y} + w\bar{x}y + \bar{w}xy$
- (c) $x\bar{y} + \bar{w}y + \bar{w}x\bar{y} + \bar{w}xy + \bar{w}x\bar{y}$
- (d) $\bar{w}xy\bar{z} + w\bar{x}y\bar{z} + \bar{w}xy\bar{z} + w\bar{x}y\bar{z} + wxy\bar{z} + \bar{w}xy\bar{z} + w\bar{x}y\bar{z} + \bar{w}x\bar{y}z$

References

- Brookshear, Brylow “An Overview of Computer Science”, 13th Ed.
- Lee “From Hardware to Software”, 1982